

Adapting ARC (Leach) Controllers for Use with HAWAI and Aladdin Arrays

Charles Lockhart
Eric Warmbier

Overview

- Main goal is to cover physical modifications made by IRTF to ARC controllers
- Intended to be a practical “How To” guide to implement the ARC controller
- Modification rationale explained
- Performance results

Controller Background

- ARC controllers are general purpose array controllers sold by Astronomical Research Cameras Inc.
 - Two sizes - 6 or 12 slot
 - Controllers configured for array type and channels
- Many observatories use ARC controllers
- IRTF uses for H2RG and Aladdin arrays
- Don Hall is presently evaluating for H4RG

ARC 32 CH H2RG Controller Setup

Video Board 3 (CH 24-31)

Video Board 2 (CH 16-23)


Video Board 1 (CH 8-15)

Video Board 0 (CH 0-7)

Bias Board (IRTF made)

Clock Driver Board

Fiber Optic Timing Board

 

Video Boards AGND normally connected to this point.
(disconnected in picture)


ARC 8 CH Aladdin Controller Setup

Video Board 0 (CH 0-7)

Clocking Board

Bias Board (IRTF made)

Fiber Optic Timing Board

 

Still testing, but most likely Bias Board won't be required and all biases will come from Clocking Board.

IRTF Modifications Table

#	Modification	H2RG	Aladdin
1	Custom Analog Bias Board	X	*
2	Video Card Ground Wires to Chassis	X	X
3	Output Source Follower RC	X	X
4	Video Board Gain Resistor Change	X	X
5	+36V Power Control Board Check Disabled	X	X
6	Bulk Capacitor on -16.5V (startup current trip)	X	**
7	Used Agilent N6700B Power Supplies	X	X

* Noise performance of Aladdin \ll H2RG, should not be required

** Aladdin uses one Video Board, startup current is much lower, not required

Mod #1: Custom Analog Bias Board

- This is the most important modification
- This solves two issues
 - Long term drift (minutes) from Video Board biases
 - Low frequency noise (<100 Hz)
- Australian National University provided their complete design as a basis to start from
 - Huge help - provided CPLD logic to control board

Mod #1: Bias Drift Reduction


- Bias drifts affects array output over long integration periods (minutes)
 - Bias drifts result in output signal drift (noise)
 - Non-destructive reads (NDRs) not as effective
- The bias board reduces drift by using
 - Low drift reference (ADR4533BRZ - 2ppm/°C max)
 - Low drift DAC (AD7568BSZ - 5 ppm FSR/°C max)
 - Low drift op-amp (OP484FSZ - 2 μ V/°C offset max)
 - Separate board = lower power and temperature

Mod #1: Low Frequency Bias Filter

- Low frequency noise present during darks
 - Appeared as banding across readout (<100 Hz)
 - Low level, but significant when dark
- Used low frequency RC filter on biases
 - VBIASPOWER and VBIASGATE most important
 - VBIASPOWER current draw is 100s of μA
 - Large R causes voltage drop due to current
 - VBIASGATE is nearly zero (gate of FET)

Mod #1: Bias Filter RCs

 2200 uF Tantalum 100 uF Ceramics 10 Ω resistor




10 Ω resistor used on other channels for commonality since impact was minor. Only VBIASGATE requires low value resistor. If too large, there is a long ramp at beginning of readout due to channel output drawing a different current and the long time constant to reach steady state.

*VBIASGATE is almost zero current. It shouldn't require a large capacitor. Why then? We installed a capacitor between VBIASPOWER and VBIASGATE on the Cryogenic Configuration Board. This was found to be a mistake and required heavy filtering on VBIASGATE to compensate for this. Since an external solution was found, we decided not to open up NSFCAM to remove it.

$f_c=6$ Hz for 2600uF $f_c=40$ Hz for 400uF

Mod #2: Video Card Ground Wires

 - Suggested by Shane Jacobson
- Reduced noise by $\sim 2-3$ ADU for dark reads
 - Didn't explore reason in detail
 - There is ground star point on power board so it shouldn't be necessary, but mod works well





Mod #3: Output Source Follower RC

- Provides current for output source follower
- Bias derived from Video Board
 - Simpler cabling if Bias Board not used for this bias
 - Array not extremely sensitive to this bias normally
- When bright objects saturated an array channel on NSFCAM, “ghosting” occurred on other channels on same Video Board due to shift in bias voltage

Mod #3: Output Source Follower RC

 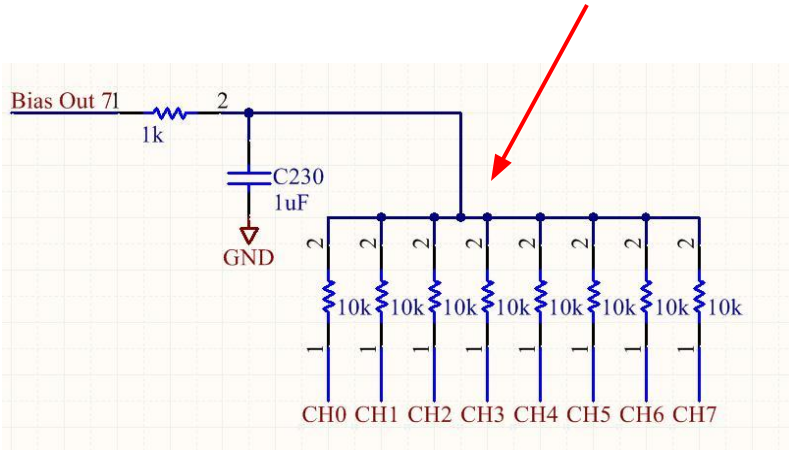There was a significant divider with 1k and 1.25k (10k/8). Current draw on channels significantly affect voltage which causes ghosting. Bias voltage is recommended to be +3.3V. Choose lower resistance value such that it forms an insignificant divider. Increase capacitor to still provide some filtering.




C357=47uF

R371=10 ohm

ARC Schematic

Mod #4: Video Board Gain Resistor

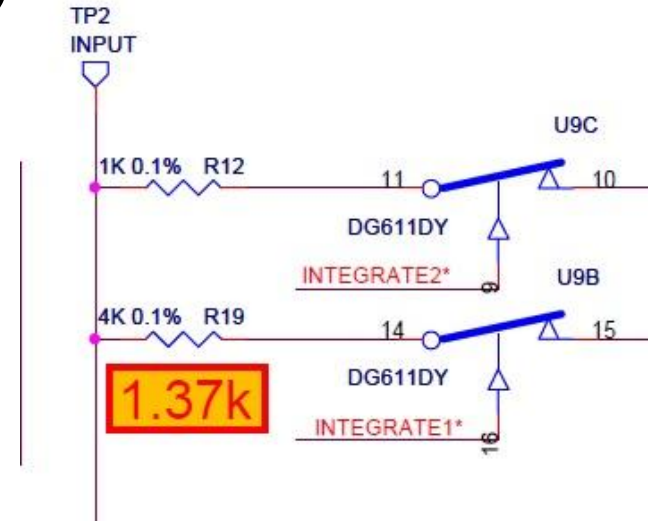- Tailored integration gain resistor for “low gain” setting (bright objects)
 - Used 1.37 k Ω
 - Maximized dynamic range
- Default 1 k Ω for high gain



Mod #5: +36V Power Check Disabled

- +36V supply is not used by H2RG or Aladdin
- Disabled +36V check
- Cut pins U5-1&2


Power Control Board



Cut


Mod #6: Bulk Capacitor on -16.5V

 - ARC controllers have no “soft start” circuitry
- Startup current high with 5 Video Boards
 - Due to charging capacitors
 - Causes overcurrent trip
- Install 6800uF(25V) cap
- Could use larger supplies
 - Cost more
 - Not necessary



Mod #7: Agilent N6700B Supplies

- High quality supplies with ethernet

 


Modules	Power Supplied
N6743B (100W)	+16.5V
N6732B (50W)	+5V Digital, +6.5V, -6.5V
N6733B (50W)	-16.5V, 12V Fan

H2RG Wiring

Channels setup differentially.
CH- is ground at Cryo PCB.

34 Channel
(twisted shielded pair)

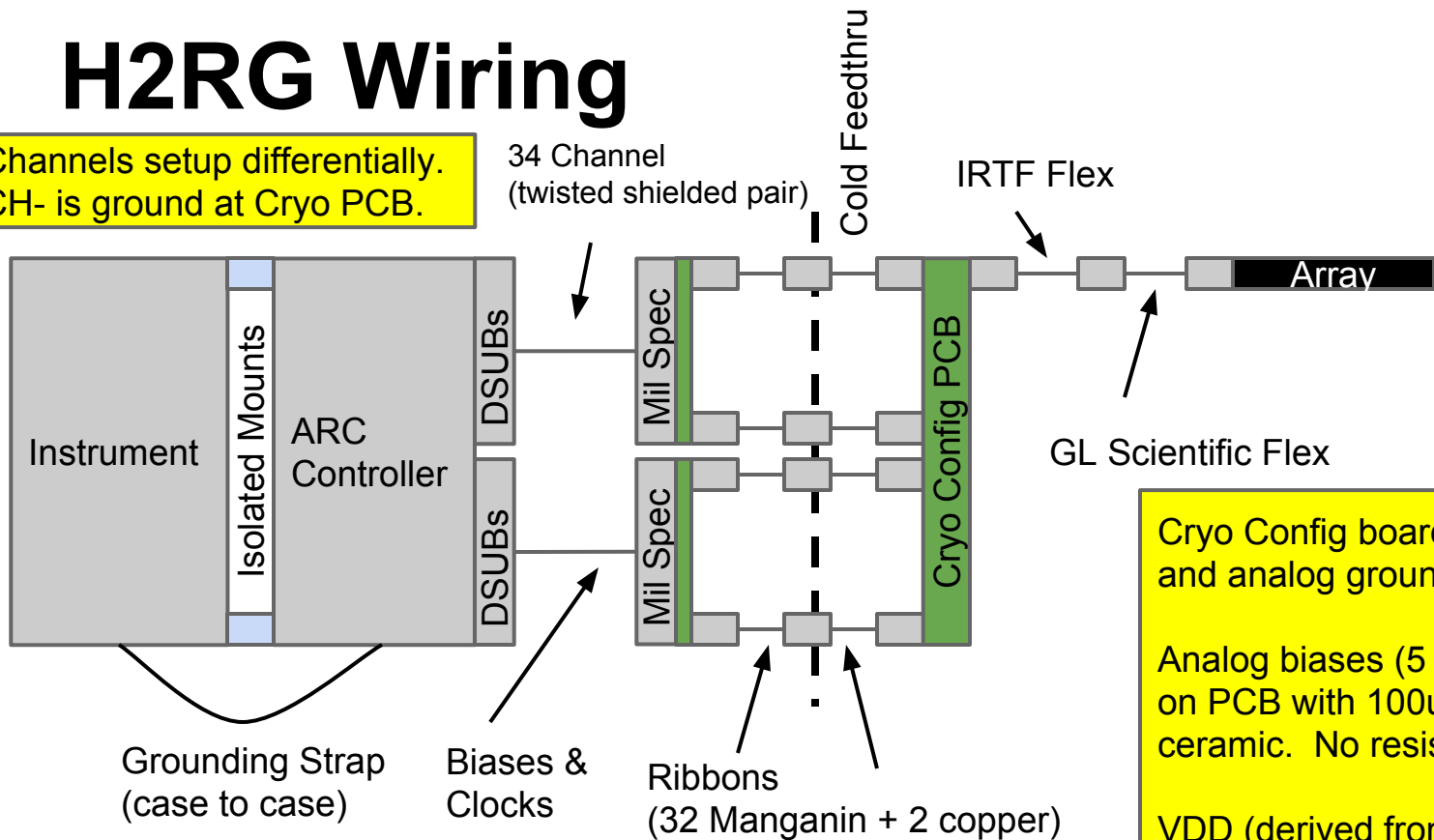

Grounding Strap
(case to case)

Biases &
Clocks

Ribbons
(32 Manganin + 2 copper)

Copper ribbon wires used for GNDs.
(for channel ribbons = windowout & ref)

IRTF Flex

GL Scientific Flex






Array

Cryo Config board keeps digital
and analog grounds separate.

Analog biases (5 total) filtered
on PCB with 100uF and 0.1uF
ceramic. No resistor.

VDD (derived from clock board)
also has 100uF and 0.1uF
capacitors. No resistor.

H2RG Wiring Hardware

     

Inside Mount

H2RG Clocking

- Clocking is fairly “standard”
- Normal pixel readout rate 200 kHz
 - Support for 100, 200, 300 kHz

H2RG Noise Results

Readout Mode	Noise Requirement	Measured	Conditions
Cryostat Standard	$\leq 15e-$	11e-	COAD=1, NDR=1
NSFCAM Standard	$\leq 15e-$	15e-	COAD=1, NDR=1
Cryostat Slow (30s)	$\leq 5e-$	3.1e-	COAD=1, NDR=16, 30s
NSFCAM Slow (30s)	$\leq 5e-$	4.4e-	COAD=1, NDR=16, 30s

- Used science grade H2RG (degraded slightly by Indium migration)
- Results obtained by selecting 40 pixel by 40 pixel area in array that was free of defective pixels
- Standard readout noise is essentially the pixel readout noise
- Slow readout using NDRs is dominated by pattern noise since it is the change in value of a pixel over a long series of readouts


Aladdin Noise Results

- Cold Aladdin readout using PAIDAI October 2013
- Results look good
- Need to verify device properties to ensure that our noise numbers are accurate before presenting

ARC H4RG Evaluation

- Don Hall is evaluating the ARC controller for the H4RG (4k x 4k) with 64 Channels
- Currently in warm mux bench test phase
- 64 channel readout successful October 2013
- Cooling down a mux in November 2013

ARC 64 CH H2RG Setup

 

Digital (Clocks) Flex

Nano Connectors

Frontplane seemed like best solution vs. wired cabling with NANO connectors.

Supports:
32 or 64 CH readout
Up to 9 Video Boards
IRTF/ANU Bias Board

Due to 8 Video Boards, stock ARC power supply is undersized. More power required.

H4RG MUX
(in a box)

Frontplane PCB
(IFA Made)

Channel & Analog
Biases Flex

WARM H4RG 64 Channel Readout

